 



Digital systems: from bits to microcontrollers

- Introduction to digital systems fundamentals
- Combinatorial digital systems
- Sequential digital systems
- Introduction to microcontrollers
- Introduction to advanced implementation platforms

Introducing state variables (internal state)





Output depends on current inputs

 

Output depends on current inputs and internal state
(which in turn depends on history of inputs)

Introducing feedback in logic elements...



Connecting output to input

  


Two stable states can be observed

Problem: how to impose a specific state?


Introducing inputs

  



Introducing inputs

 

 
Input R (reset) forces output Q to go 0;
Input S (set) forces output Q to go 1;
Outputs Q and /Q present complementary values




Introducing inputs

  

Introducing inputs

 


SR Latch

 

SR Latch

$$Q_{t+\delta} = S + \neg R \cdot Q_t = \neg(\neg S \cdot \neg(\neg R \cdot Q_t))$$
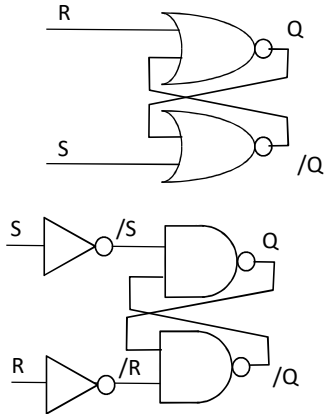
$$Q_{t+\delta} = \neg R \cdot (S + Q_t) = \neg(R + \neg(S + Q_t))$$





S	R	Q _t	Q _{t+δ}	/Q _{t+δ}
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	X	X
1	1	1	X	X

S	R	Q _{t+δ}	/Q _{t+δ}
0	0	Q _t	/Q _t
0	1	0	1
1	0	1	0
1	1	X	X

Q _{t+δ}	S			
	0	0	X	1
Q _t	1	0	X	1
	R			
Q _{t+δ}	0	0	X	1
Q _t	1	0	X	1
	R			


SR Latch with enable (gated SR latch)

  

EN	S	R	Q _{t+δ}	/Q _{t+δ}
0	-	-	Q _t	/Q _t
1	0	0	Q _t	/Q _t
1	0	1	0	1
1	1	0	1	0
1	1	1	X	X


S	R	Q _{t+δ}	/Q _{t+δ}
0	0	Q _t	/Q _t
0	1	0	1
1	0	1	0
1	1	X	X

Delay (D) Latch with enable

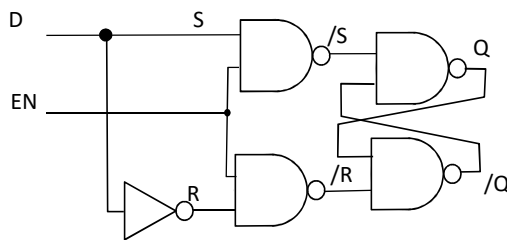


EN	D	$Q_{t+\delta}$	$/Q_{t+\delta}$
0	-	Q_t	$/Q_t$
1	0	0	1
1	1	1	0

Introducing master-slave flip-flop

 


new data into the master

 

input gates disable

data moved from the master to the slave


Introducing master-slave flip-flop

 

SR truth table

S	R	Q_{n+1}	$/Q_{n+1}$
0	0	Q_n	$/Q_n$
0	1	0	1
1	0	1	0
1	1	x	x

Introducing master-slave JK flip-flop

 

JK truth table

J	K	Q_{n+1}	$/Q_{n+1}$
0	0	Q_n	$/Q_n$
0	1	0	1
1	0	1	0
1	1	$/Q_n$	Q_n

Master-slave versus edge-triggered flip-flops


While:

- master-slave flip-flop are receptive to inputs during one level of the clock and updates output in one edge of the clock,
- edge-triggered flip-flops are receptive to inputs in the same clock edge where output are updated.



In this sense, the edge-triggered flip-flop truth table applies considering the inputs at the moment immediately before the clock edge.

Edge-triggered flip-flops are the ones normally used.


Most common flip-flops

 


Asynchronous inputs: active values

  

 
May I use one flip-flop to produce a different one?



D	Q_{n+1}
0	0
1	1

 


J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$/Q_n$

 


T	Q_{n+1}
0	Q_n
1	$/Q_n$

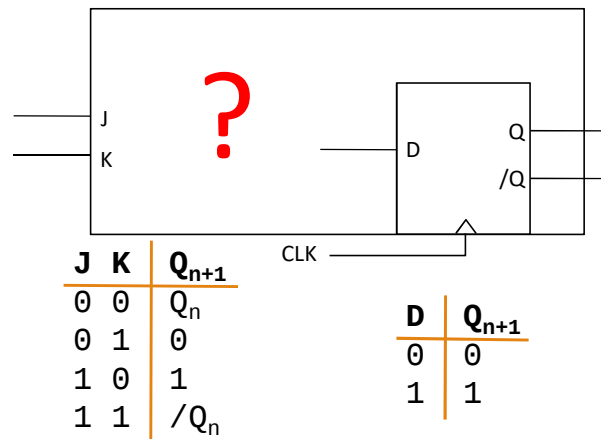May I use one D flip-flop to produce a JK flip-flop?



May I use one D flip-flop to produce a JK flip-flop?

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 


May I use one D flip-flop to produce a JK flip-flop?

J	K	Q_n	Q_{n+1}	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

$Q_n \rightarrow Q_{n+1}$	D
0 → 0	0
0 → 1	1
1 → 0	0
1 → 1	1

D	Q_{n+1}
0	0
1	1

 


May I use one D flip-flop to produce a JK flip-flop?


J	K	Q_n	Q_{n+1}	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

	J	
	0	1
Q_n	1	0
	K	
	0	1
Q_n	1	0
 
$$D = J \cdot \neg Q_n + \neg K \cdot Q_n$$




 Flip-flop truth tables and transition tables




Connecting flip-flops into registers

 
A group of flip-flops using the same synchronizing signal is a register.




A shift-register

 

Left and right shift-registers

 

Left-right shift-register

 


If (SEL = 0) then shift left
else shift right

Shift-registers as counters: ring counter



N flips => N counting states

CLK						
	↑		↑		↑	
$Q_0 = D_1$	1	0	0	1	0	0
$Q_1 = D_2$	0	1	0	0	1	0
$Q_2 = D_0$	0	0	1	0	0	1

 



Shift-registers as counters: twisted-ring counter (Johnson counter)

  N flips $\Rightarrow 2 \cdot N$ counting states



A simple counter



J	K	Q _{n+1}
0	0	Q _n
0	1	0
1	0	1
1	1	/Q _n

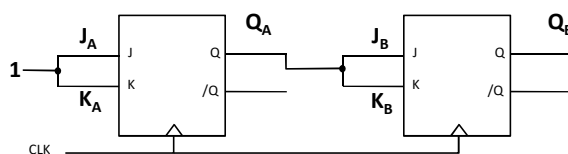 

(Q_B Q_A) 00 01 10 11 00 01
0 1 2 3 0 1

N flips $\Rightarrow 2^N$ counting states
2-bit counter (modulo 4)


A 2^n counter ($n=3$)

 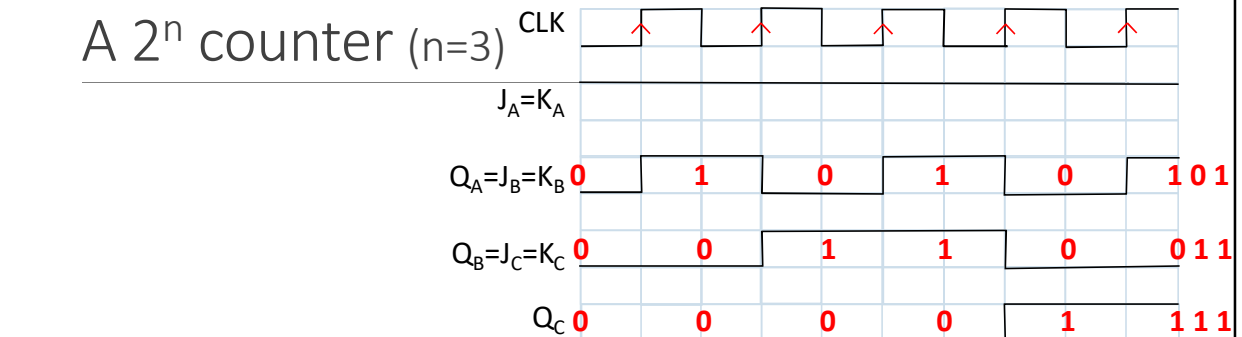

Revisiting registers

Sometimes is necessary that one register performs different functions along the time.

 
As the flip-flop structure is the same for all functions, the different functions are implemented through different flip-flop input functions.




Revisiting registers

Sometimes is necessary that one register performs different functions along the time.

 As the flip-flop structure is the same for all functions, the different functions are implemented through different flip-flop input functions.




Left-right shift-register

 


If (SEL = 0) then shift left
else shift right

Register with parallel load control

 


If ($\text{LOAD} = 1$) then load data inputs
else freeze outputs

Register with parallel load control

 


If ($\text{LOAD} = 1$) then load data inputs
else freeze outputs

 Register with parallel load control and clear




If ($\text{LOAD} = 1$) then load data inputs
 else if ($\text{CLEAR} = 1$) then clear outputs
 else freeze outputs

 Register with parallel load control and clear



If ($\text{LOAD} = 1$) then load data inputs
 else if ($\text{CLEAR} = 1$) then clear outputs
 else freeze outputs

 Register with parallel load control and clear



If (CLEAR = 1) then clear outputs
 else if (LOAD = 1) then load data inputs
 else freeze outputs

An arbitrary modulus counter

$0 \rightarrow 1 \rightarrow 2 \rightarrow 0 \rightarrow 1 \rightarrow \dots$

For example: modulus 3 counter

An arbitrary modulus counter

0 → 1 → 2 → 0 → 1 → ...


Current state	Next state
$S_i = Q_1 Q_0$	
$S_0 = 00$	$S_1 = 01$
$S_1 = 01$	$S_2 = 10$
$S_2 = 10$	$S_0 = 00$

An arbitrary modulus counter (modulus 3)


0 → 1 → 2 → 0 → 1 → ...

$$S_i = Q_1 Q_0$$


Current state	Next state
$(Q_1 Q_0)_n$	$(Q_1 Q_0)_{n+1} \quad D_1 D_0$
$(S_0) \ 0 \ 0$	$0 \ 1 \quad 0 \ 1$
$(S_1) \ 0 \ 1$	$1 \ 0 \quad 1 \ 0$
$(S_2) \ 1 \ 0$	$0 \ 0 \quad 0 \ 0$

 

$$D1 = Q0$$

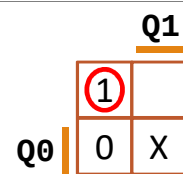



$$D0 = /Q1 ./ Q0 = /(Q1 + Q0)$$

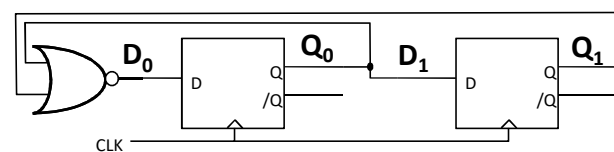

A modulus 3 counter

$$S_i = Q_1 Q_0$$


Current state	Next state	
$(Q_1 Q_0)_n$	$(Q_1 Q_0)_{n+1}$	$D_1 D_0$
$(S_0) 0 0$	0 1	0 1
$(S_1) 0 1$	1 0	1 0
$(S_2) 1 0$	0 0	0 0

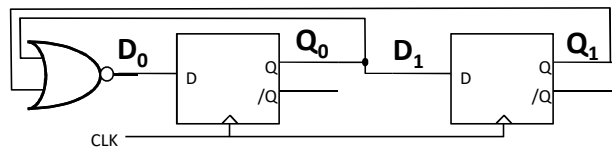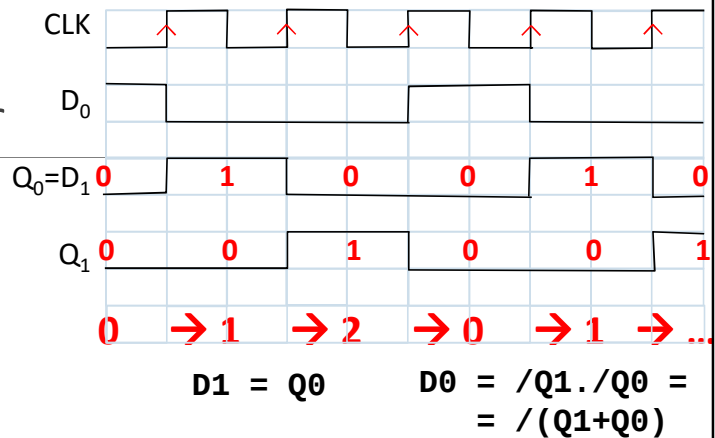

Up-down counter

For example: modulus 3 up/down counter

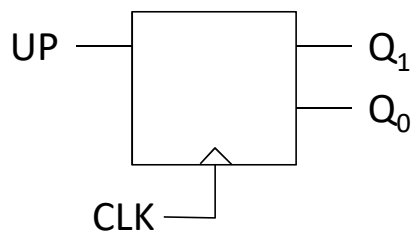if (UP = 1) then counts up
else counts down



Modulus 3 up/down counter

if (UP = 1) then counts up
else counts down

$$S_i = Q_1 Q_0$$

Current state ($Q_1 Q_0$) _n	Next state	
	UP=0 ($Q_1 Q_0$) _{n+1}	UP=1 ($Q_1 Q_0$) _{n+1}
(S ₀) 0 0	1 0	0 1
(S ₁) 0 1	0 0	1 0
(S ₂) 1 0	0 1	0 0

Current state			Next state	
UP ($Q_1 Q_0$) _n			($Q_1 Q_0$) _{n+1}	
0	0	0	1	0
0	0	1	0	0
0	1	0	0	1
0	1	1	X	X
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	X	X

Modulus 3 up/down counter

if (UP = 1) then counts up
else counts down

$$S_i = Q_1 Q_0$$

Current state ($Q_1 Q_0$) _n	Next state		FF inputs	
	UP=0 ($Q_1 Q_0$) _{n+1}	UP=1 ($Q_1 Q_0$) _{n+1}	UP=0 D ₁ D ₀	UP=1 D ₁ D ₀
(S ₀) 0 0	1 0	0 1	1 0	0 1
(S ₁) 0 1	0 0	1 0	0 0	1 0
(S ₂) 1 0	0 1	0 0	0 1	0 0
1 1	X X	X X	X X	X X


UP			
D ₁	1	0	0
Q _{0n}	0	X	1
Q _{1n}			
UP			
D ₀	0	1	0
Q _{0n}	0	X	0
Q _{1n}			

Modulus 3 up/down counter

if (UP = 1) then counts up
else counts down

$$S_i = Q_1 Q_0$$


Current state ($Q_1 Q_0$) _n	Next state	
	UP=0 ($Q_1 Q_0$) _{n+1}	UP=1 ($Q_1 Q_0$) _{n+1}
(S ₀) 0 0	1 0	0 1
(S ₁) 0 1	0 0	1 0
(S ₂) 1 0	0 1	0 0

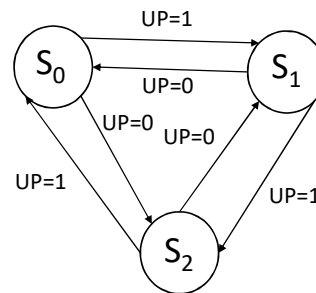


Sequence detectors

Consider transmitting binary information through a communication channel. The data is transmitted synchronously with a clock signal, at a specific rate.

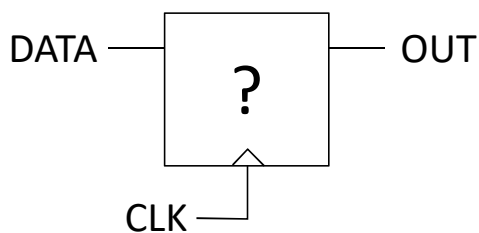
We intend to produce a system, which will analyze the data transmitted and detects whenever a specific sequence occurs.



Sequence detector for 100

 


Brief comment on notation

 

Moore state machine


Outputs associated with states

 

Mealy state machine

Outputs associated with transitions

 Sequence detector for 100: using Moore state machine




S_0 – out of sequence

S_1 – detected first bit of the sequence

S_2 – detected two first bits of the sequence

S_3 – sequence detected

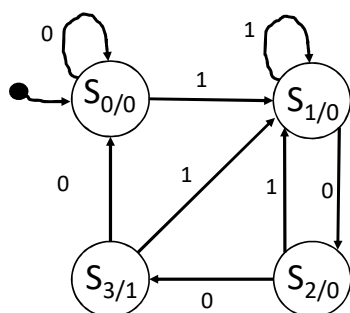Sequence detector for 100: using Moore state machine



Current state	Next state		OUT
	DATA=0	DATA=1	
S_0	S_0	S_1	0
S_1	S_2	S_1	0
S_2	S_3	S_1	0
S_3	S_0	S_1	1

1 – State diagram

2 – State transition table and outputs

Sequence detector for 100: using Moore state machine

Current state	$Q_1 Q_0$
S_0	0 0
S_1	0 1
S_2	1 0
S_3	1 1

3 – State encoding

Current state $(Q_1 Q_0)_n$	Next state		OUT
	DATA=0 $(Q_1 Q_0)_{n+1}$	DATA=1 $(Q_1 Q_0)_{n+1}$	
(S_0) 00	00	01	0
(S_1) 01	10	01	0
(S_2) 10	11	01	0
(S_3) 11	00	01	1

4 – Encoded state transition table and outputs

Sequence detector for 100: using Moore state machine

$Q_1 \rightarrow$ flip-flop D

$Q_0 \rightarrow$ flip-flop D

(or any others)

5 – Selection of flip-flops


D	Q_{n+1}
0	0
1	1

$Q_n \rightarrow Q_{n+1}$	D
0 0	0
0 1	1
1 0	0
1 1	1


Current state $(Q_1 Q_0)_n$	Next state		Flip-flop inputs		Outputs OUT
	DATA=0 $(Q_1 Q_0)_{n+1}$	DATA=1 $(Q_1 Q_0)_{n+1}$	DATA=0 $D_1 D_0$	DATA=1 $D_1 D_0$	
(S_0) 00	00	01	00	01	0
(S_1) 01	10	01	10	01	0
(S_2) 10	11	01	11	01	0
(S_3) 11	00	01	00	01	1

6 – Determining flip-flops input functions and output functions

 Sequence detector for 100: using Moore state machine



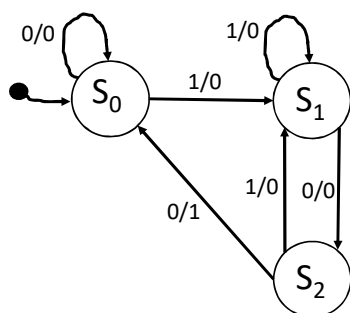Sequence detector for 100: using Mealy state machine




S₀ – out of sequence

S₁ – detected first bit of the sequence

S₂ – detected two first bits of the sequence

 Sequence detector for 100: using Mealy state machine




1 – State diagram

Current state	Next state		OUT	
	DATA=0	DATA=1	DATA=0	DATA=1
S ₀	S ₀	S ₁	0	0
S ₁	S ₂	S ₁	0	0
S ₂	S ₀	S ₁	1	0


2 – State transition table and outputs

Sequence detector for 100: comparing Moore and Mealy state machines

Moore specification

 


Mealy specification

 


Development methodology for synchronous state machines

- 1 – Draw the state diagram describing desired behavior
- 2 – Draw state transition table and outputs
- 3 – State encoding
- 4 – Encoded state transition table and outputs
- 5 – Selection of flip-flops
- 6 – Determining flip-flops input functions and output functions
- 7 – Simplification of functions (namely using Karnaugh maps)
- 8 – Schematic
- 9 – Simulation, implementation and tests

 
Reference architecture for execution/implementation



 
Sequence detector for 100 using shift register



 Sequence detector for 100 using shift register



 Sequence detector for 100 using shift register



Mealy output