


Digital systems: from bits to microcontrollers

- Introduction to digital systems fundamentals
- Combinatorial digital systems
- Sequential digital systems
- Introduction to microcontrollers
- Introduction to advanced implementation platforms

Revisiting registers

Sometimes is necessary that one register performs different functions along the time.

 
As the flip-flop structure is the same for all functions, the different functions are implemented through different flip-flop input functions.




Revisiting registers

Sometimes is necessary that one register performs different functions along the time.

 As the flip-flop structure is the same for all functions, the different functions are implemented through different flip-flop input functions.




Left-right shift-register

 


If (SEL = 0) then shift left
else shift right

Register with parallel load control

 


If (LOAD = 1) then load data inputs
else freeze outputs

Register with parallel load control

 


If (LOAD = 1) then load data inputs
else freeze outputs

 Register with parallel load control and clear




If (LOAD = 1) then load data inputs
 else if (CLEAR = 1) then clear outputs
 else freeze outputs

 Register with parallel load control and clear



If (LOAD = 1) then load data inputs
 else if (CLEAR = 1) then clear outputs
 else freeze outputs

 Register with parallel load control and clear




If (CLEAR = 1) then clear outputs
 else if (LOAD = 1) then load data inputs
 else freeze outputs

Coping with data processing dominated systems → FSM with Datapaths

Finite State Machine ← “Control-dominated”

Finite State Machine
 cooperative with data
 processing architecture ← “Data-processing-dominated”

 
→ Partitioning the system
 into control part
 and datapath




A simple multiplier

Goal: to implement one multiplier of one number (with N bits) by 3.


Strategy: Result = $0 + A + A + A$

 

 
A $3 \cdot A$ multiplier ($C = 0 + A + A + A$)




A 3*A multiplier ($C = 0+A+A+A$)

 

A 3*A multiplier ($C = 0+A+A+A$)

 


A 3*A multiplier ($C = 0+A+A+A$)

 


A 3*A multiplier ($C = 0+A+A+A$)

 - wait for GO=1
- Clear RC
- Add A
- Add A
- Add A
- Wait for GO=0



A 3*A multiplier ($C = 0 + A + A + A$)

 


Exercise: multiplier of two numbers

Goal: to implement one multiplier of two numbers
(with N bits each).

One multiplier (I)

 Goal: to implement one multiplier of two numbers (with N bits each), using successive additions algorithm.



$$C = A \times B$$


↓

$$C = \underbrace{0 + A + A + \dots + A}_{B \text{ times}}$$

One multiplier (II)

Datapath based on a Register Transfer Level architecture

 
→ Successive additions, using add-and-accumulate register to store partial additions as well as final result



One multiplier (II)

Datapath based on a Register Transfer Level architecture

 
- Successive additions, using add-and-accumulate register to store partial additions as well as final result
- What about B times counter?



One multiplier (III)

Datapath: counting B times:


Option 1 - using an up-counter

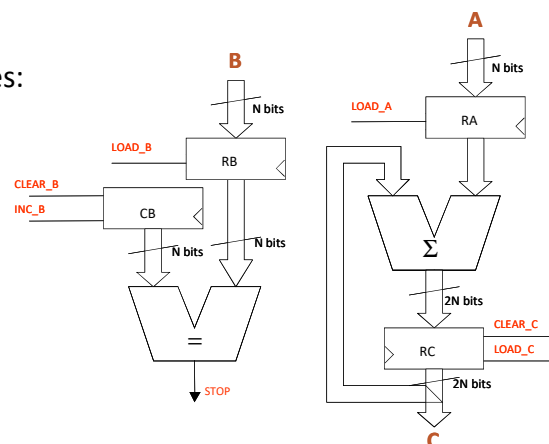

One multiplier (IV)


Datapath: counting B times

Option 2 - using a down-counter

 


One multiplier (V)


Control part

 


FSM with Datapath

 


Introducing tri-state buffers

 


Introducing tri-state buffers

 

Introducing buses

 


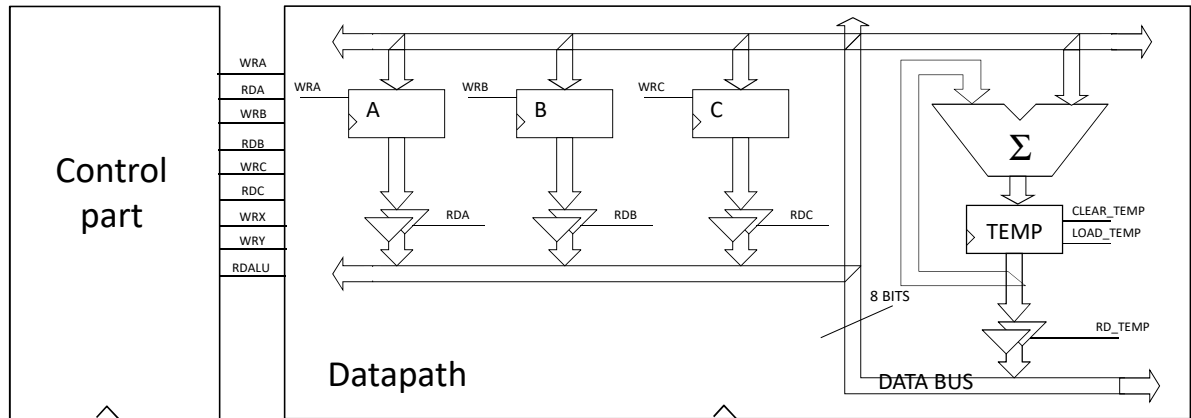Control sequence to compute $A \leftarrow 2*B + A + C$




Control sequence to compute $A \leftarrow 2*B + A + C$ ($A \leftarrow B + B + A + C$)

 Copy B to TEMP
 Accumulate B on TEMP
 Accumulate A on TEMP
 Accumulate C on TEMP
 Copy TEMP to A




Control sequence to compute $A \leftarrow 2*B+A+C$ ($A \leftarrow B+B+A+C$)

 Clear TEMP
 Accumulate B on TEMP
 Accumulate B on TEMP
 Accumulate A on TEMP
 Accumulate C on TEMP
 Copy TEMP to A




 Control sequence to compute $A \leftarrow 2*B+A+C$ ($A \leftarrow B+B+A+C$)




Clear TEMP
 Accumulate B on TEMP
 Accumulate B on TEMP
 Accumulate A on TEMP
 Accumulate C on TEMP
 Copy TEMP to A

 
Control sequence to compute $A \leftarrow 2*B + A + C$ ($A \leftarrow B + B + A + C$)



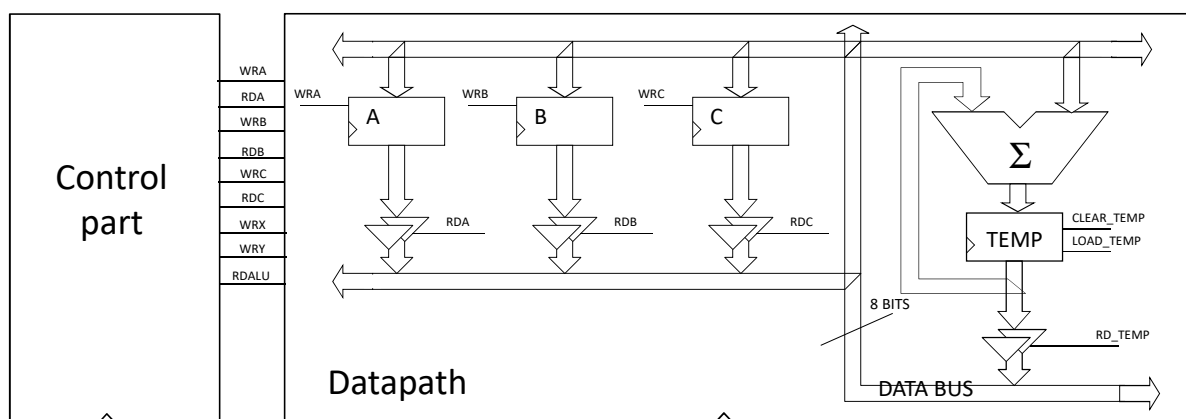
Control sequence to compute $A \leftarrow 2*(B+A) + 3*C$



Connecting to the external world

 

 Moving from dedicated architectures to general purpose microprocessor architectures



Introducing memories

Unit: BIT (BIrary digiT)



- 1 Byte = 8 Bits
- 1 K (Kilobyte) = $2^{10} = 1024$
- 1 M (Megabyte) = $2^{20} = 1\,048\,576$
- 1 G (Gigabyte) = $2^{30} = 1\,073\,741\,824$
- 1 T (Terabyte) = $2^{40} = 1\,099\,511\,627\,776$
- 1 P (Petabyte) = $2^{50} = 1\,125\,899\,906\,842\,624$

Different technologies available for solid state memories


ROM	Read-Only Memory
PROM	Programmable Read-Only Memory
EPROM	Erasable Programmable Read-Only Memory
EEPROM	Electrically Erasable Programmable Read-Only Memory

RAM	Random Access Memory
SRAM	Static Random Access Memory
DRAM	Dynamic Random Access Memory

...

  


ROM structure

 


Address	Data
0	011
1	111
2	010
3	110

Using a ROM to implement a function

 

Address	$A_1 A_0$	Data
0	00	011
1	01	111
2	10	010
3	11	110

Using a ROM to implement a function

 

$$F_2(A,B) = \Sigma(1,3)$$


$$F_1(A,B) = \Sigma(0,1,2,3)$$

$$F_0(A,B) = \Sigma(0,1)$$


A	B	F ₂	F ₁	F ₀
00	0	1	1	1
01	1	1	1	1
10	0	1	0	0
11	1	1	0	0

A ₁ A ₀	D ₂	D ₁	D ₀
00	0	1	1
01	1	1	1
10	0	1	0
11	1	1	0

Using a ROM to implement a function

 


Address lines
A₁A₀

 

D₂D₁D₀
Data out lines

A ₁ A ₀	D ₂	D ₁	D ₀
00	0	1	1
01	1	1	1
10	0	1	0
11	1	1	0


RAM structure

 


Revisiting how to implement combinatorial functions?

- Simplification using Karnaugh maps or Quine-McCluskey methods
- Direct implementation:
 - Using decoders + additional logic
 - Using multiplexers
 - Using memories

A simple microcontroller

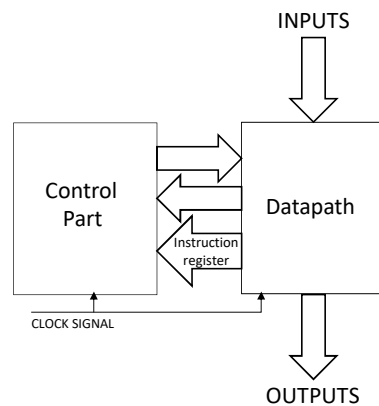

The datapath

 

Instruction set

IR7	IR6	IR5	IR4	IR3	IR2	IR1	IR0	Instructions
0	0	0	0	-	-	-	-	HALT
0	0	0	1	-	-	-	-	CLEAR TEMP
0	0	1	0	-	n	-	m	IN FROM n TO m
0	0	1	1	-	-	-	m	STORE TEMP TO m
0	1	0	0	-	-	-	m	ADD m TO TEMP
0	1	0	1	-	-	-	m	SUB m TO TEMP
0	1	1	0	-	-	-	m	LOAD TEMP WITH m
0	1	1	1	-	n	-	m	OUT FROM M TO n

The datapath

Instructions

HALT

CLEAR TEMP

IN FROM n TO m


STORE TEMP TO m

ADD m TO TEMP

SUB m TO TEMP

LOAD TEMP WITH m

OUT FROM M TO n

 

$$OUT_A = 2 * IN_A - IN_B$$

Instructions

HALT

CLEAR TEMP

IN FROM n TO m


STORE TEMP TO m

ADD m TO TEMP

SUB m TO TEMP


LOAD TEMP WITH m

OUT FROM m TO n

 

$$OUT_A = 2 * IN_A - IN_B$$

 IN FROM IN_A TO REG_A
 LOAD TEMP WITH REG_A
 ADD REG_A TO TEMP
 IN FROM IN_B TO REG_A
 SUB REG_A TO TEMP
 STORE TEMP TO REG_A
 OUT FROM REG_A TO OUT_A
 HALT




OUT_A =
2*IN_A-IN_B

IR7	IR6	IR5	IR4	IR3	IR2	IR1	IR0	Instructions
0	0	0	0	-	-	-	-	HALT
0	0	0	1	-	-	-	-	CLEAR TEMP
0	0	1	0	-	n	-	m	IN FROM n TO m
0	0	1	1	-	-	-	m	STORE TEMP TO m
0	1	0	0	-	-	-	m	ADD m TO TEMP
0	1	0	1	-	-	-	m	SUB m TO TEMP
0	1	1	0	-	-	-	m	LOAD TEMP WITH m
0	1	1	1	-	n	-	m	OUT FROM M TO n


Instruction code

0 0 1 0 - 0 - 0 IN FROM IN_A TO REG_A
 0 1 1 0 - - - 0 LOAD TEMP WITH REG_A
 0 1 0 0 - - - 0 ADD REG_A TO TEMP
 0 0 1 0 - 1 - 0 IN FROM IN_B TO REG_A
 0 1 0 1 - - - 0 SUB REG_A TO TEMP
 0 0 1 1 - - - 0 STORE TEMP TO REG_A
 0 1 1 1 - 0 - 0 OUT FROM REG_A TO OUT_A
 0 0 0 0 - - - - HALT


OUT_A =
2*IN_A-IN_B

 

OUT_B =
3*IN_B-2*IN_A ?

 


A simple microcontroller

 


The control part

 
Fetch the instruction code
Decode &
Execution the instruction




The datapath

 


Control part - initialization

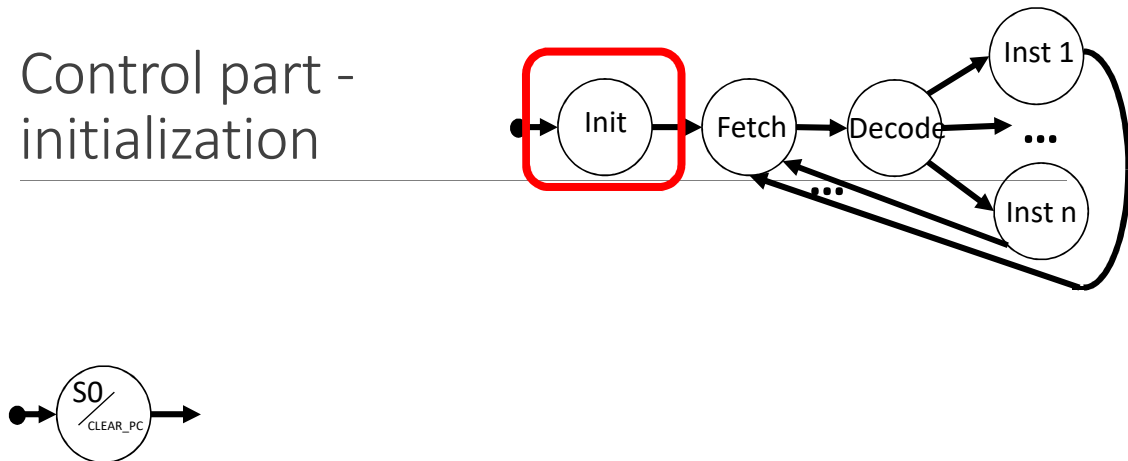


Control part - fetch

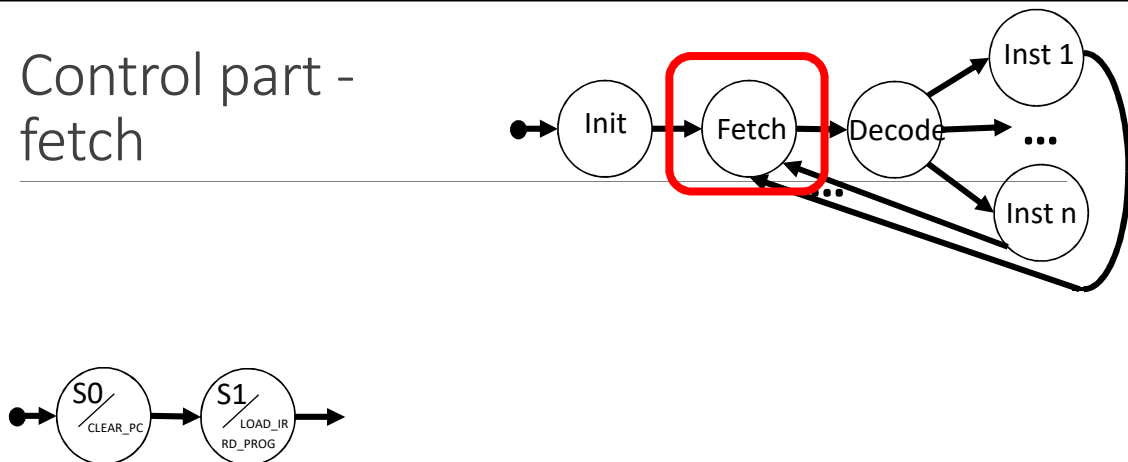


Control part - decode

 


Control part – execute HALT

 


Control part – execute LOAD

 


Control part – execute ADD

 


Control part – execute ADD

 

Implementing the control part

 

A simple microcontroller

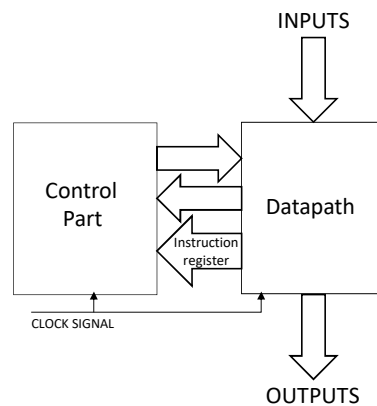

A simple microcontroller

Instructions

HALT
 CLEAR TEMP
 IN FROM n TO m
 STORE TEMP TO m
 ADD m TO TEMP
 SUB m TO TEMP
 LOAD TEMP WITH m
 OUT FROM m TO n

