


Digital systems: from bits to microcontrollers

- Introduction to digital systems fundamentals
- Combinatorial digital systems
- Sequential digital systems
- Introduction to microcontrollers
- Introduction to advanced implementation platforms

Revisiting registers

Sometimes is necessary that one register performs different functions along the time.

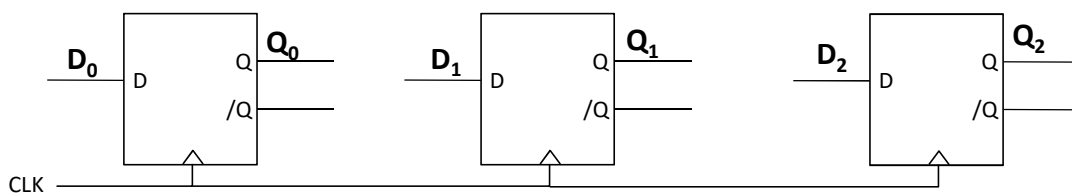
As the flip-flop structure is the same for all functions, the different functions are implemented through different flip-flop input functions.




Revisiting registers

Sometimes is necessary that one register performs different functions along the time.

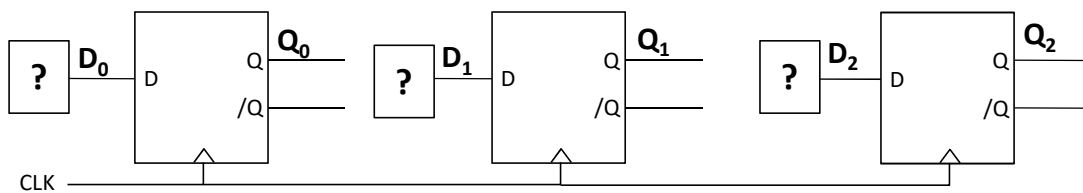As the flip-flop structure is the same for all functions, the different functions are implemented through different flip-flop input functions.




Left-right shift-register

 


If (SEL = 0) then shift left
else shift right

Register with parallel load control

 


If (LOAD = 1) then load data inputs
else freeze outputs

Register with parallel load control

 


If (LOAD = 1) then load data inputs
else freeze outputs

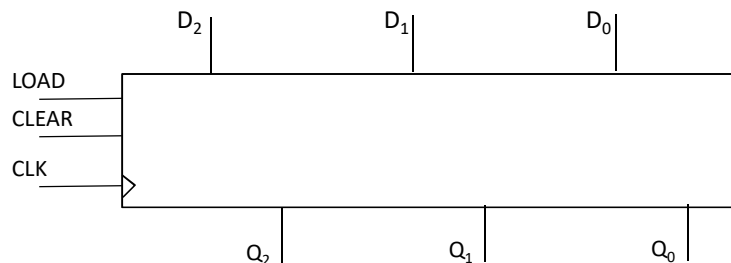Register with parallel load control and clear




If (LOAD = 1) then load data inputs
 else if (CLEAR = 1) then clear outputs
 else freeze outputs

 Register with parallel load control and clear



If (LOAD = 1) then load data inputs
 else if (CLEAR = 1) then clear outputs
 else freeze outputs

 Register with parallel load control and clear




If (CLEAR = 1) then clear outputs
 else if (LOAD = 1) then load data inputs
 else freeze outputs

Coping with data processing dominated systems → FSM with Datapaths

Finite State Machine ← “Control-dominated”

Finite State Machine
 cooperative with data
 processing architecture ← “Data-processing-dominated”

 
→ Partitioning the system
 into control part
 and datapath




A simple multiplier

Goal: to implement one multiplier of one number (with N bits) by 3.


Strategy: Result = $0 + A + A + A$

 

 
A $3 \cdot A$ multiplier ($C = 0 + A + A + A$)




A 3*A multiplier ($C = 0+A+A+A$)

 

A 3*A multiplier ($C = 0+A+A+A$)

 


A 3*A multiplier ($C = 0+A+A+A$)

 


A 3*A multiplier ($C = 0+A+A+A$)

 - wait for GO=1
- Clear RC
- Add A
- Add A
- Add A
- Wait for GO=0



A 3*A multiplier ($C = 0+A+A+A$)

 


Exercise: multiplier of two numbers

Goal: to implement one multiplier of two numbers (with N bits each).

One multiplier (I)

 Goal: to implement one multiplier of two numbers (with N bits each), using successive additions algorithm.



$$C = A \times B$$


↓

$$C = \underbrace{0 + A + A + \dots + A}_{B \text{ times}}$$

One multiplier (II)

Datapath based on a Register Transfer Level architecture

 
→ Successive additions, using add-and-accumulate register to store partial additions as well as final result



One multiplier (II)

Datapath based on a Register Transfer Level architecture

 
- Successive additions, using add-and-accumulate register to store partial additions as well as final result
- What about B times counter?



One multiplier (III)

Datapath: counting B times:


Option 1 - using an up-counter

 

One multiplier (IV)


Datapath: counting B times

Option 2 - using a down-counter

 

One multiplier (V)

Control part

 

FSM with Datapath

